



K21U 2073

Reg. No. :

Name :

**III Semester B.Sc. Degree (CBCSS – Sup./Imp.) Examination, November 2021
(2015 – '18 Admissions)
GENERAL COURSE IN COMPUTER SCIENCE
3A12CSC : Digital Electronics**

Time : 3 Hours

Max. Marks : 40

SECTION – A

1. **One** word answer. **(8×0.5=4)**
- a) 2's complement of the binary number 10110100_2 is _____
 - b) The base of hexadecimal number system is _____
 - c) For a two input XOR gate we get a high output if _____
 - d) A _____ has single input and many outputs.
 - e) In a seven segment display, LEDs b and c lit up. Then the decimal number displayed is _____
 - f) Condition for JK flip flop to toggle is _____
 - g) If a counter is connected using 6 flip flop then the maximum number of states that the counter count is _____
 - h) In sequential circuits the output states depend upon _____.

SECTION – B

Write short notes on **any seven** of the following questions. **(7×2=14)**

- 2. Find the binary and BCD equivalent of the decimal number 2469.
- 3. State de-Morgan's first law.
- 4. State associative law for Boolean addition.
- 5. Define cell adjacency in k-map.
- 6. Why are multiplexers called data selectors ?

P.T.O.



7. What is the function of a decoder ?
8. Define flip flop.
9. What is a master slave flip flop ?
10. Define a sequential circuit.
11. Give an account of shift register counter.

SECTION – C

Answer **any four** of the following questions.

(4×3=12)

12. Convert $Y = A + BC' + AB + A'BC$ into canonical form.
13. Explain the advantages and disadvantages of k-map method.
14. List the difference between combinational and sequential circuits.
15. Give the comparison between synchronous and asynchronous counters.
16. Minimize the function $f = x(y + w'z) + wxz$ using Boolean algebra.
17. Define the two types of shift register counters.

SECTION – D

Write an essay on **any two** of the following questions.

(2×5=10)

18. With suitable examples explain the methods for implementing signed arithmetic.
 19. Simplify the expression $F(A, B, C, D) = \sum(5, 7, 8, 9, 13, 15)$ using Karnaugh map. Draw the logic diagram of the expression both before and after simplifying.
 20. With relevant figure and waveform explain SR, D and JK flip flops.
 21. Design a four bit magnitude comparator which checks for equality, less than and greater than conditions.
-