



**K21U 1110**

Reg. No. : .....

Name : .....

**IV Semester B.Sc. Degree CBCSS (OBE) Regular Examination, April 2021  
(2019 Admission Only)  
General Awareness Course in Computer Science  
4A13CSC : DIGITAL ELECTRONICS**

Time : 3 Hours

Max. Marks : 40

**PART – A  
(Short Answer)**

Answer **all** questions.

**(6×1=6)**

1. What is an analog system ?
2. Give the digital waveform.
3. What is XOR gate principle ?
4. Define Octet.
5. What is a parallel adder ?
6. Give an example for a sequential circuit.

**PART – B  
(Short Essay)**

Answer **any six** questions.

**(6×2=12)**

7. Explain Gray Code.
8. Give the truth table of OR Gate.
9. Draw XNOR Gate.
10. What is NOT Operation ?
11. Demonstrate how NAND gate used as a AND gate.
12. Give an example for a parallel counter. What is its function ?
13. What is an asynchronous counter ? Give an example.
14. What are latches ? Explain.

P.T.O.




## PART – C

## (Essay)

Answer **any four** questions.

(4×3=12)

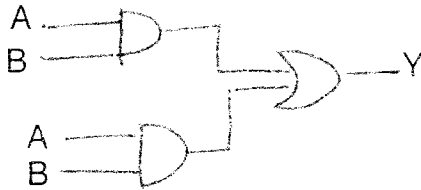15. Convert Binary (1111) to decimal.
16. Convert decimal 6754 to octal.
17. Construct truth table for



18. Explain Encoder and Decoder.
19. What is a Full Adder ?
20. Compare synchronous and asynchronous counters.

## PART – D

## (Long Essay)

Answer **any two** questions.

(2×5=10)

21. Convert 1) Octal 1234 to Binary 2) Hexadecimal ABCD to decimal.
22. Draw circuit for

$Y = (\bar{A} + B + C)(A - B + \bar{C})$  Use Boolean Algebra to simplify. Draw corresponding logic circuit.

23. Explain Master Slave Flip Flop.
  24. Explain the different number systems.
-