



K21U 4562

Reg. No. : .....

Name : .....

V Semester B.Sc. Degree CBCSS (OBE) Regular  
Examination, November 2021  
(2019 Admn. Only)  
CORE COURSE IN PHYSICS  
5B09PHY : Electronics – II

Time : 3 Hours

Max. Marks : 40

SECTION – A

(Very short answer type. Answer **all** questions. **Each** question carries **1** mark.)

1. What do you mean by operating point ?
2. The purpose of a coupling capacitor in transistor amplifier is
3. Write down the expression for frequency of Colpitt's Oscillator.
4. The inputs to an XOR Gate is 1 and 1. What is its output ?
5. A differential amplifier has a common mode gain of 0.3 and a differential voltage gain of 3000. Determine CMRR.
6. An inverting amplifier has  $R_i = 10 \text{ K}\Omega$  and  $R_f = 100 \text{ K}\Omega$ . The closed loop voltage gain is  
(6×1=6)

SECTION – B

(Short essay type. Answer **any 6** questions. **Each** question carries **2** marks.)

7. Explain De Morgan's theorem with an example.
8. Differentiate open loop and closed loop voltage gain.
9. Explain the working of an inverting amplifier.
10. Write a short note on hybrid parameters and their dimensions.

P.T.O.



11. What is a Phase shift oscillator ? Draw the circuit and obtain the expression for frequency.
12. Express power gain and voltage gain in decibel unit. What is the importance of expressing gain in decibel unit ?
13. Explain the following terms :
  - 1) Frequency Response
  - 2) Band width.
14. Illustrate Sum of Products method with an example. (6×2=12)

## SECTION – C

(Problem type. Answer **any 4** questions. **Each** question carries **3** marks.)

15. Obtain an expression for the closed loop voltage gain of a non-inverting amplifier.
16. Calculate the operating frequency and feedback fraction of Hartley oscillator. Given  $L_1 = 1$  mH,  $L_2 = 0.1$  mH,  $C = 20$  pF. The mutual inductance between coils is 0.02 mH. Calculate the feedback fraction.
17. Draw a full adder circuit. Obtain the expression for sum and carry.
18. For a single stage CE transistor amplifier circuit  $R_1 = 10$  K $\Omega$ ,  $R_2 = 5$  K $\Omega$ ,  $R_C = 1$  K $\Omega$ ,  $R_E = 2$  K $\Omega$ ,  $R_L = 1$  K $\Omega$ ,  $V_{BE} = 0.7$  V and  $V_{CC} = 15$  V.
  - 1) Draw the dc load line.
  - 2) Determine the operating point.
  - 3) Draw the ac load line.
19. Simplify the Boolean expression  $X = AB + A(B + C) + B(B + C)$ .
20. Convert the SOP expression  $X = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + ABC$  to POS. (4×3=12)

## SECTION – D

(Long essay type. Answer **any 2** questions. **Each** question carries **5** marks.)

21. Draw the circuit of a single stage common emitter transistor amplifier. Explain the functions of all components and show that output is 180° out of phase with the input.
22. What is a power amplifier ? Compare Class A, Class B and Class C amplifiers.
23. Explain the working of an integrator and a differentiator circuit using Op-amp.
24. Briefly explain the working of comparator, decoder and encoder circuits. (2×5=10)