



K24U 0715

Reg. No. :

Name :

IV Semester B.Sc. Degree (CBCSS – OBE – Regular/Supplementary/
Improvement) Examination, April 2024


(2019 to 2022 Admissions)

GENERAL AWARENESS COURSE IN COMPUTER SCIENCE

4A13CSC : Digital Electronics

Time : 3 Hours

Max. Marks : 40

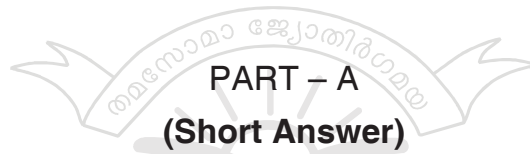


PART – A

(Short Answer)

Answer **all** questions.

(6×1=6)

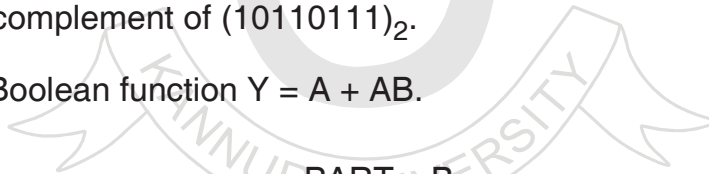1. What is the BCD representation of the decimal number 12 ?
2. Give truth table of a NAND gate.
3. Which logic gates are known as Universal Gates ?
4. Explain the purpose of Flip-flops in digital circuits ?
5. Give the 1's complement of $(10110111)_2$.
6. Simplify the Boolean function $Y = A + AB$.



PART – B

(Short Essay)

Answer **any six** questions.

(6×2=12)

7. Convert $(427)_{10}$ to Hexadecimal.
8. State De-Morgan's Theorem.
9. Draw the Combinational Circuit of a Half Adder.
10. Give any two differences between Latches and Flip-flops.

P.T.O.



11. Explain Gray Code.
12. Apply De-Morgan's Theorem and reduce the Boolean Function $Y = \overline{ABC}$.
13. Differentiate Multiplexers and Demultiplexers.
14. Differentiate Combinational Circuits and Sequential Circuits.

PART – C

(Essay)

Answer **any four** questions.

(4×3=12)

15. Write note on ASCII and UNICODE.
16. What are SOP and POS expression formats ?
17. What are Parity Generators ? What is its role in Digital Data Transmission ?
18. Explain the working of JK Flip-flop with suitable diagram.
19. Draw the sequential circuit for a 4 bit asynchronous counter.
20. Design a 4 to 2 Encoder.

PART – D

(Long Essay)

Answer **any two** questions.

(2×5=10)

21. Explain with an example how binary subtraction can be performed using 1's and 2's complement addition.
 22. Minimize the following Boolean function using K-Map
 $OF(A, B, C, D) = \sum m(0, 1, 3, 5, 7, 8, 9, 11, 13, 15)$.
 23. Realise the universal property of any one of the Universal Gate.
 24. Explain various Shift Registers in detail.
-